

# Homework 3


CSM51A 2019 Summer

Due to July 24 (Wednesday) 8 PM

Submit your homework on CCLE using HW3 submission link

1. Show that the set {XNOR, OR} is universal. You can use constant 0 or 1 (only one of them).

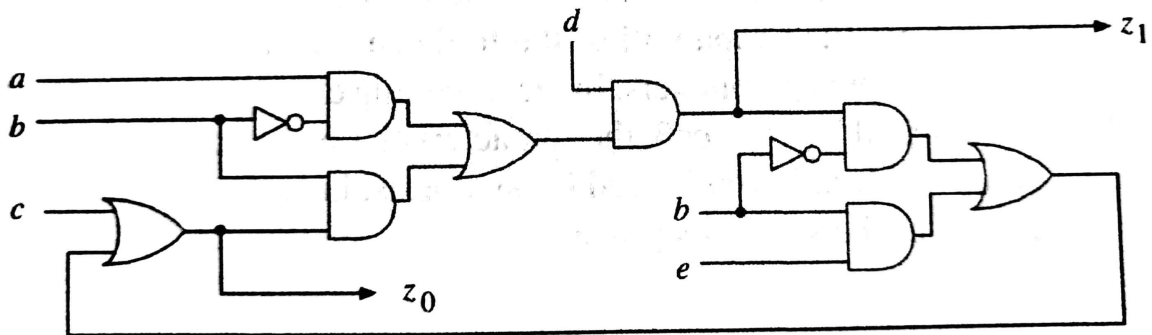2. Show that the network in the figure below is combinational even though there is a physical loop.



3. Represent on K-maps the functions described by the following expressions

$$(1) E(x, y, z) = \Sigma m(1, 5, 7)$$

$$(2) E(w, x, y, z) = w'x'y + y'z + xz'$$

4. For  $f(w, x, y, z) = \text{one\_set}(0, 1, 2, 3, 5, 7, 8, 10, 11, 15)$

(1) Find all the prime implicants.

(2) Indicate which of these prime implicants are essential.

(3) Obtain a minimal sum of products for  $f$ . Is it unique?

5. Design a minimal two-level NOR network that performs a code conversion from the four-bit binary to the four-bit Gray code. Minimize each output expression separately using K-maps.